



Звіт

З лабораторної роботи № 3

З дисципліни «Моделювання комп'ютерних систем»

На тему: «Поведінковий опис цифрового автомата. Перевірка роботи автомата за допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант: 14

Виконав: ст. гр. КІ-202

Лесяк Х. В.

Прийняв:

Козак Н. Б.

Львів – 2023

Мета: Поведінковий опис цифрового автомата. Перевірка роботи автомата за допомогою стенда Elbert V2 – Spartan 3A FPGA

Варіант:

ВАРІАНТ	ВИРАЗ
0	$((OP1 - OP2) + 4) \ll OP2$

Виконання роботи

Реалізував елементи за допомогою мови опису VHDL

RAM.vhdl

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 16:49:14 04/27/2023  
-- Design Name:  
-- Module Name: RAM - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity RAM_intf is
port(
    RAM_WR                : IN STD_LOGIC;
    RAM_ADDR_BUS          : IN STD_LOGIC_VECTOR(1
downto 0);
    ACC_DATA_IN_BUS       : IN STD_LOGIC_VECTOR(7 downto 0);
    RAM_DATA_OUT_BUS: OUT STD_LOGIC_VECTOR(7 downto
0);
    CLOCK                : IN STD_LOGIC
    );
end RAM_intf;

architecture RAM_arch of RAM_intf is
type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
signal RAM_UNIT          : ram_type;
signal RAM_DATA_IN_BUS   : STD_LOGIC_VECTOR(7 downto 0);

```

```

begin
    RAM_DATA_IN_BUS <= ACC_DATA_IN_BUS;

    RAM : process(CLOCK, RAM_ADDR_BUS, RAM_UNIT)
    begin
        if (rising_edge(CLOCK)) then
            if (RAM_WR = '1') then
                RAM_UNIT(conv_integer(RAM_ADDR_BUS)) <=
RAM_DATA_IN_BUS;
            end if;
        end if;

        RAM_DATA_OUT_BUS <=
RAM_UNIT(conv_integer(RAM_ADDR_BUS));
    end process RAM;

end RAM_arch;

```

ALU.VHDL

```

-----

-- Company:
-- Engineer:
--
-- Create Date: 16:13:46 04/27/2023
-- Design Name:
-- Module Name: ALU - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:

```

--

-- Dependencies:

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

use IEEE.NUMERIC_STD.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx primitives in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity ALU_intf is

port(

 IN_SEL_OUT_BUS : IN STD_LOGIC_VECTOR(7 downto 0);

 ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7 downto 0);

 OP_CODE_BUS : IN STD_LOGIC_VECTOR(1 downto 0);

 ACC_DATA_IN_BUS : OUT STD_LOGIC_VECTOR(7 downto 0);

 OVER_FLOW : OUT STD_LOGIC

 --OF - overflow

```
);  
end ALU_intf;
```

architecture ALU_arch of ALU_intf is

begin

```
ALU : process(OP_CODE_BUS, IN_SEL_OUT_BUS, ACC_DATA_OUT_BUS)
```

```
    variable A : unsigned(7 downto 0);
```

```
    variable B : unsigned(7 downto 0);
```

```
    variable temp : std_logic_vector(8 downto 0);
```

```
begin
```

```
    A := unsigned(ACC_DATA_OUT_BUS);
```

```
    B := unsigned(IN_SEL_OUT_BUS);
```

```
    if OP_CODE_BUS = "00" then
```

```
        ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(B);
```

```
    elsif OP_CODE_BUS = "01" then
```

```
        temp := STD_LOGIC_VECTOR('0' & A) +  
STD_LOGIC_VECTOR('0' & B);
```

```
        if (temp(8) = '1') then
```

```
            OVER_FLOW <= '1';
```

```
        else
```

```
            OVER_FLOW <= '0';
```

```
        end if;
```

```
        ACC_DATA_IN_BUS <= temp(7 downto 0);
```

```
    elsif OP_CODE_BUS = "10" then
```

```
        temp := STD_LOGIC_VECTOR('0' & A) -  
STD_LOGIC_VECTOR('0' & B);
```

```
        if (temp(8) = '1') then
```

```
            OVER_FLOW <= '1';
```

```

else

    OVER_FLOW <= '0';

    end if;

    ACC_DATA_IN_BUS <= temp(7 downto 0);

elseif OP_CODE_BUS = "11" then
    case(B) is --case(B) is
        when x"00"    => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 0);
        when x"01"    => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 1);
        when x"02"    => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 2);
        when x"03"    => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 3);
        when x"04"    => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 4);
        when x"05"    => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 5);
        when x"06"    => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 6);
        when x"07"    => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 7);
        when others => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 0);
    end case;

else

    ACC_DATA_IN_BUS <= "00000000";

    end if;

end process ALU;

```

end ALU_arch;

MUX.vhdl

-- Company:

-- Engineer:

--

-- Create Date: 15:06:55 04/27/2023

-- Design Name:

-- Module Name: MUX - Behavioral

-- Project Name:

-- Target Devices:

-- Tool versions:

-- Description:

--

-- Dependencies:

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

use IEEE.NUMERIC_STD.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;


```

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity MUX_intf is
    port(
        DATA_IN          : IN STD_LOGIC_VECTOR(7 downto 0);
        CONSTANT_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
        RAM_DATA_OUT_BUS: IN STD_LOGIC_VECTOR(7 downto 0);
        IN_SEL              : IN STD_LOGIC_VECTOR(1
downto 0);
        IN_SEL_OUT_BUS : OUT std_logic_vector(7 downto 0)
    );
end MUX_intf;

architecture MUX_arch of MUX_intf is

begin
    INSEL_A_MUX : process(DATA_IN, CONSTANT_BUS,
RAM_DATA_OUT_BUS, IN_SEL)
        begin
            if(IN_SEL = "00") then
                IN_SEL_OUT_BUS <= DATA_IN;
            elsif(IN_SEL = "01") then
                IN_SEL_OUT_BUS <= RAM_DATA_OUT_BUS;
            else
                IN_SEL_OUT_BUS <= CONSTANT_BUS;
            end if;
        end process;
    end architecture;

```

```
        end if;

        end process INSEL_A_MUX;

end MUX_arch;
```

ACC.vhdl

```
-----

-- Company:
-- Engineer:
--
-- Create Date: 15:27:57 04/27/2023
-- Design Name:
-- Module Name: ACC - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
```

```
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
```

```

use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity ACC_intf is
port(
    CLOCK          : IN STD_LOGIC;
    ACC_RST        : IN STD_LOGIC;
    ACC_WR         : IN STD_LOGIC;
    ACC_DATA_IN_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
    ACC_DATA_OUT_BUS : OUT STD_LOGIC_VECTOR(7 downto
0)
    );
end ACC_intf;

architecture ACC_arch of ACC_intf is

signal ACC_DATA          : STD_LOGIC_VECTOR(7 downto 0);

begin
    ACC : process(CLOCK, ACC_DATA)
    begin
        if (rising_edge(CLOCK)) then
            if(ACC_RST = '1') then
                ACC_DATA <= "00000000";
            end if;
        end if;
    end process;
end ACC_arch;

```

```

        elsif (ACC_WR = '1') then
            ACC_DATA <= ACC_DATA_IN_BUS;
        end if;
    end if;
    ACC_DATA_OUT_BUS <= ACC_DATA;
end process ACC;
end ACC_arch;

```

SEGDEC.vhdl

```

-----

-- Company:
-- Engineer:
--
-- Create Date: 17:15:15 04/27/2023
-- Design Name:
-- Module Name: SEGDEC - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;

```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx primitives in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
entity SEGDEC_intf is
```

```
port(
```

```
    CLOCK          : IN STD_LOGIC;
```

```
    ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
```

```
    RESET          : IN STD_LOGIC;
```

```
    OverFlow_IN : IN STD_LOGIC;
```

```
    COMM_ONES     : OUT STD_LOGIC;
```

```
    COMM_DECS     : OUT STD_LOGIC;
```

```
    COMM_HUNDREDS : OUT STD_LOGIC;
```

```
    SEG_A         : OUT STD_LOGIC;
```

```
    SEG_B         : OUT STD_LOGIC;
```

```
    SEG_C         : OUT STD_LOGIC;
```

```
    SEG_D         : OUT STD_LOGIC;
```

```
    SEG_E         : OUT STD_LOGIC;
```

```
    SEG_F         : OUT STD_LOGIC;
```

```
    SEG_G         : OUT STD_LOGIC;
```

```
    DP            : OUT STD_LOGIC;
```

```

        OverFlow_OUT : OUT STD_LOGIC := '0'

    );

end SEGDEC_intf;

architecture SEGDEC_arch of SEGDEC_intf is
    signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
    signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
    signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
begin

```

```

OVERFLOW_INDICATE : process(OverFlow_IN, RESET)
    begin
        --if rising_edge(CLOCK) then
            if (RESET = '1') then
                OverFlow_OUT <= '0';
            elsif (RESET = '0' and OverFlow_IN = '1') then
                OverFlow_OUT <= '1';
            end if;
        --end if;
    end process OVERFLOW_INDICATE;

```

```

BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
    variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
    variable bcd      : STD_LOGIC_VECTOR(11 downto 0) ;
begin
    bcd      := (others => '0') ;
    hex_src  := ACC_DATA_OUT_BUS;

```

```

for i in hex_src'range loop
    if bcd(3 downto 0) > "0100" then
        bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
    end if ;
    if bcd(7 downto 4) > "0100" then
        bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
    end if ;
    if bcd(11 downto 8) > "0100" then
        bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
    end if ;

    bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new
entry
    hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; -- shift src
+ pad with 0
end loop ;

```

```

HONDREDS_BUS    <= bcd (11 downto 8);

```

```

DECS_BUS        <= bcd (7 downto 4);

```

```

ONES_BUS        <= bcd (3 downto 0);

```

```

end process BIN_TO_BCD;

```

```

INDICATE : process(CLOCK)

```

```

    type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

```

```

    variable CUR_DIGIT    : DIGIT_TYPE := ONES;

```

```

    variable DIGIT_VAL    : STD_LOGIC_VECTOR(3 downto 0) :=
"0000";

```

```

variable DIGIT_CTRL    : STD_LOGIC_VECTOR(6 downto 0) :=
"0000000";

variable COMMONS_CTRL : STD_LOGIC_VECTOR(2 downto 0)
:= "000";

begin

    if (rising_edge(CLOCK)) then
        if(RESET = '0') then
            case CUR_DIGIT is
                when ONES =>
                    DIGIT_VAL := ONES_BUS;
                    CUR_DIGIT := DECS;
                    COMMONS_CTRL := "001";
                when DECS =>
                    DIGIT_VAL := DECS_BUS;
                    CUR_DIGIT := HUNDREDS;
                    COMMONS_CTRL := "010";
                when HUNDREDS =>
                    DIGIT_VAL := HONDREDS_BUS;
                    CUR_DIGIT := ONES;
                    COMMONS_CTRL := "100";
                when others =>
                    DIGIT_VAL := ONES_BUS;
                    CUR_DIGIT := ONES;
                    COMMONS_CTRL := "000";
            end case;

            case DIGIT_VAL is          --abcdefg
                when "0000" => DIGIT_CTRL :=
"1111110";

```



```

when "0001" => DIGIT_CTRL :=
"0110000";

when "0010" => DIGIT_CTRL :=
"1101101";

when "0011" => DIGIT_CTRL :=
"1111001";

when "0100" => DIGIT_CTRL :=
"0110011";

when "0101" => DIGIT_CTRL :=
"1011011";

when "0110" => DIGIT_CTRL :=
"1011111";

when "0111" => DIGIT_CTRL :=
"1110000";

when "1000" => DIGIT_CTRL :=
"1111111";

when "1001" => DIGIT_CTRL :=
"1111011";

when others => DIGIT_CTRL := "0000000";

end case;

else
    DIGIT_VAL := ONES_BUS;
    CUR_DIGIT := ONES;
    COMMONS_CTRL := "000";
end if;

COMM_ONES    <= COMMONS_CTRL(0);
COMM_DECS    <= COMMONS_CTRL(1);
COMM_HUNDREDS <= COMMONS_CTRL(2);

SEG_A <= DIGIT_CTRL(6);

```

```
SEG_B <= DIGIT_CTRL(5);
SEG_C <= DIGIT_CTRL(4);
SEG_D <= DIGIT_CTRL(3);
SEG_E <= DIGIT_CTRL(2);
SEG_F <= DIGIT_CTRL(1);
SEG_G <= DIGIT_CTRL(0);
DP    <= '0';
```

```
end if;
```

```
end process INDICATE;
```

```
end SEGDEC_arch;
```

CU.vhdl

```
-----
-- Company:
-- Engineer:
--
-- Create Date: 16:27:31 04/27/2023
-- Design Name:
-- Module Name: CU - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
```

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

use IEEE.NUMERIC_STD.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx primitives in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity CU_intf is

 port(CLOCK : IN STD_LOGIC;

 RESET : IN STD_LOGIC;

 ENTER_OP1 : IN STD_LOGIC;

 ENTER_OP2 : IN STD_LOGIC;

 CALCULATE : IN STD_LOGIC;

 RAM_WR : OUT STD_LOGIC;

 RAM_ADDR_BUS : OUT STD_LOGIC_VECTOR(1 downto 0);

 CONSTANT_BUS : OUT STD_LOGIC_VECTOR(7 downto
0):= "00000100";

 ACC_WR : OUT STD_LOGIC;

 ACC_RST : OUT STD_LOGIC;

 IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);

```

        OP_CODE_BUS : OUT STD_LOGIC_VECTOR(1 downto 0)

    );

end CU_intf;

architecture CU_arch of CU_intf is

    type cu_state_type is (cu_rst, cu_idle, cu_load_op1, cu_load_op2, cu_run_calc0,
        cu_run_calc1, cu_run_calc2, cu_run_calc3, cu_finish);

    signal cu_cur_state : cu_state_type;
    signal cu_next_state : cu_state_type;

begin
    CONSTANT_BUS      <= "00000100";
    CU_SYNC_PROC: process (CLOCK)
    begin
        if (rising_edge(CLOCK)) then
            if (RESET = '1') then
                cu_cur_state <= cu_rst;
            else
                cu_cur_state <= cu_next_state;
            end if;
        end if;
    end process;

    CUNEXT_STATE_DECODE: process (cu_cur_state, ENTER_OP1,
        ENTER_OP2, CALCULATE)
    begin
        --declare default state for next_state to avoid latches
        cu_next_state <= cu_cur_state; --default is to stay in current state
    end process;
end architecture CU_arch;

```

--insert statements to decode next_state

--below is a simple example

```
case(cu_cur_state) is
    when cu_rst          =>
        cu_next_state <= cu_idle;
    when cu_idle          =>
        if (ENTER_OP1 = '1') then
            cu_next_state <= cu_load_op1;
        elsif (ENTER_OP2 = '1') then
            cu_next_state <= cu_load_op2;
        elsif (CALCULATE = '1') then
            cu_next_state <= cu_run_calc0;
        else
            cu_next_state <= cu_idle;
        end if;
    when cu_load_op1      =>
        cu_next_state <= cu_idle;
    when cu_load_op2      =>
        cu_next_state <= cu_idle;
    when cu_run_calc0 =>
        cu_next_state <= cu_run_calc1;
    when cu_run_calc1 =>
        cu_next_state <= cu_run_calc2;
    when cu_run_calc2 =>
        cu_next_state <= cu_run_calc3;
    when cu_run_calc3 =>
        cu_next_state <= cu_finish;
    when cu_finish       =>
        cu_next_state <= cu_finish;
```

```

        when others          =>
            cu_next_state <= cu_idle;
    end case;
end process;

```

CU_OUTPUT_DECODE: process (cu_cur_state)

begin

case(cu_cur_state) is

```

    when cu_rst          =>
        IN_SEL           <= "00";
        OP_CODE_BUS     <= "00";
        RAM_ADDR_BUS    <= "00";
        RAM_WR          <= '0';
        ACC_RST         <= '1';
        ACC_WR          <= '0';

    when cu_idle         =>
        IN_SEL           <= "00";
        OP_CODE_BUS     <= "00";
        RAM_ADDR_BUS    <= "00";
        RAM_WR          <= '0';
        ACC_RST         <= '0';
        ACC_WR          <= '0';

    when cu_load_op1     =>
        IN_SEL           <= "00";
        OP_CODE_BUS     <= "00";
        RAM_ADDR_BUS    <= "00";
        RAM_WR          <= '1';
        ACC_RST         <= '0';

```

```

        ACC_WR                <= '1';

when cu_load_op2 =>
    IN_SEL                    <= "00";
    OP_CODE_BUS <= "00";
    RAM_ADDR_BUS <= "01";
    RAM_WR                <= '1';
    ACC_RST                <= '0';
    ACC_WR                <= '1';

when cu_run_calc0 => --get op1 to accumulator
    IN_SEL                    <= "01"; --mux
    OP_CODE_BUS <= "00"; --operation
    RAM_ADDR_BUS <= "00"; --digit adress
    RAM_WR                <= '0'; -- write to ram
    ACC_RST                <= '0'; -- reset accumulator
    ACC_WR                <= '1'; -- write accumulator

when cu_run_calc1 =>
    IN_SEL                    <= "01";
    OP_CODE_BUS <= "10";
    RAM_ADDR_BUS <= "01";
    RAM_WR                <= '0';
    ACC_RST                <= '0';
    ACC_WR                <= '1';

when cu_run_calc2 =>
    IN_SEL                    <= "11";
    OP_CODE_BUS <= "01";
    RAM_ADDR_BUS <= "01";
    RAM_WR                <= '0';
    ACC_RST                <= '0';
    ACC_WR                <= '1';

```

```

when cu_run_calc3 =>
    IN_SEL          <= "01";
    OP_CODE_BUS    <= "11";
    RAM_ADDR_BUS   <= "01";
    RAM_WR         <= '0';
    ACC_RST        <= '0';
    ACC_WR         <= '1';
when cu_finish     =>
    IN_SEL          <= "00";
    OP_CODE_BUS    <= "00";
    RAM_ADDR_BUS   <= "00";
    RAM_WR         <= '0';
    ACC_RST        <= '0';
    ACC_WR         <= '0';
when others        =>
    IN_SEL          <= "00";
    OP_CODE_BUS    <= "00";
    RAM_ADDR_BUS   <= "00";
    RAM_WR         <= '0';
    ACC_RST        <= '0';
    ACC_WR         <= '0';
end case;
end process;
end CU_arch;

```

Створила елементи для кожного файлу та зібрала у єдину схему TopLevel

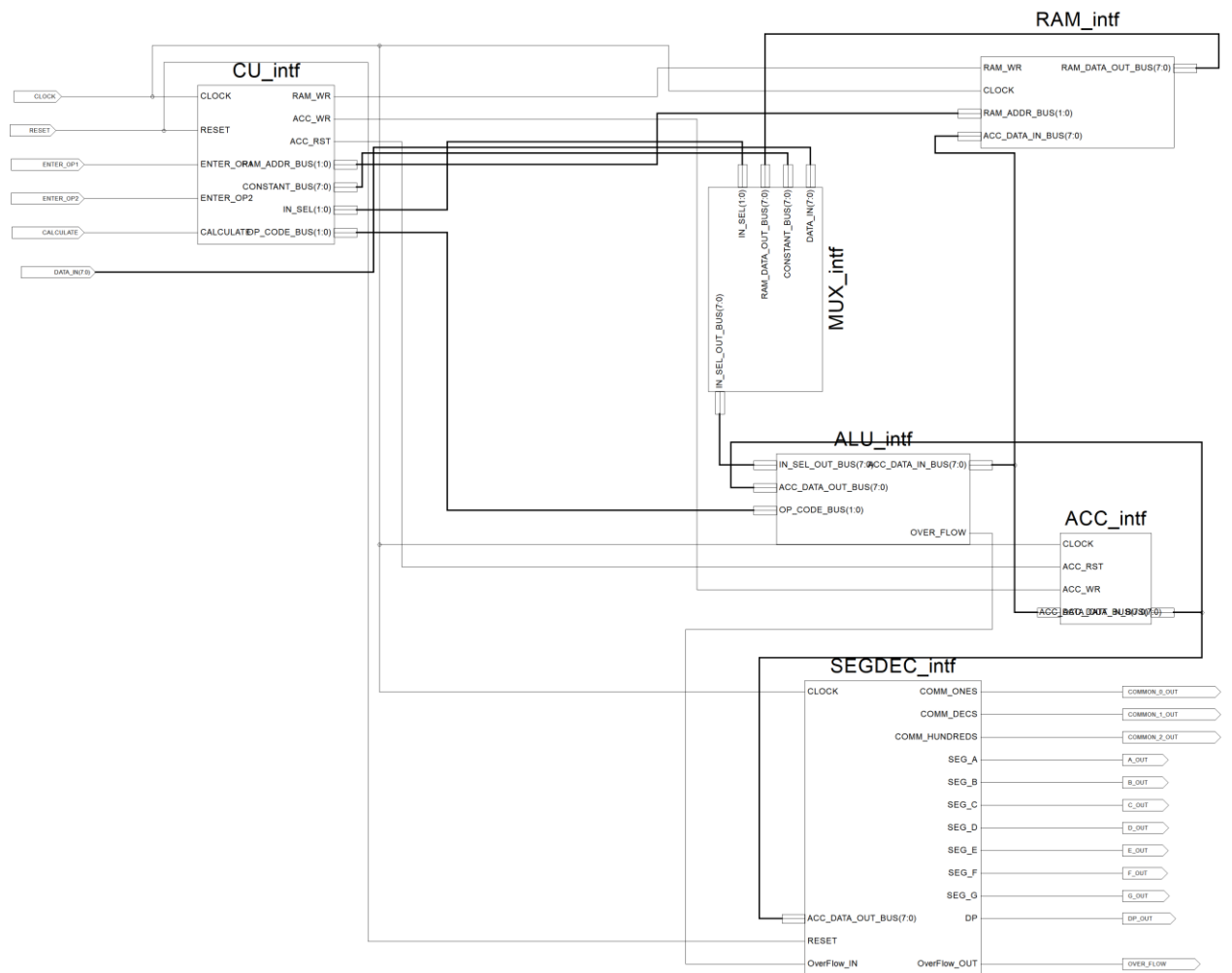


Рис.1 – TopLevel.sch

Створила файл симуляції для зручного дослідження схеми

-- Vhdl test bench created from schematic D:\Lab_3_Example\TopLevel.sch

--

-- Notes:

-- 1) This testbench template has been automatically generated using types

-- std_logic and std_logic_vector for the ports of the unit under test.

-- Xilinx recommends that these types always be used for the top-level

-- I/O of a design in order to guarantee that the testbench will bind

-- correctly to the timing (post-route) simulation model.

-- 2) To use this template as your testbench, change the filename to any

-- name of your choice with the extension .vhd, and use the "Source->Add"

```
-- menu in Project Navigator to import the testbench. Then
-- edit the user defined section below, adding code to generate the
-- stimulus for your design.
```

```
--
```

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
USE ieee.numeric_std.ALL;
```

```
LIBRARY UNISIM;
```

```
USE UNISIM.Vcomponents.ALL;
```

```
ENTITY TopLevel_TopLevel_sch_tb IS
```

```
END TopLevel_TopLevel_sch_tb;
```

```
ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS
```

```
    COMPONENT TopLevel
```

```
    PORT( RESET   :    IN    STD_LOGIC;
```

```
          ENTER_OP1   :    IN    STD_LOGIC;
```

```
          ENTER_OP2   :    IN    STD_LOGIC;
```

```
          CALCULATE   :    IN    STD_LOGIC;
```

```
          COMMON_0_OUT :    OUT STD_LOGIC;
```

```
          COMMON_1_OUT :    OUT STD_LOGIC;
```

```
          COMMON_2_OUT :    OUT STD_LOGIC;
```

```
          A_OUT       :    OUT STD_LOGIC;
```

```
          B_OUT       :    OUT STD_LOGIC;
```

```
          C_OUT       :    OUT STD_LOGIC;
```

```
          D_OUT       :    OUT STD_LOGIC;
```

```
          E_OUT       :    OUT STD_LOGIC;
```

```
          F_OUT       :    OUT STD_LOGIC;
```

```
          G_OUT       :    OUT STD_LOGIC;
```

```
          DP_OUT      :    OUT STD_LOGIC;
```

```
CLOCK      :      IN      STD_LOGIC;
DATA_IN    :      IN      STD_LOGIC_VECTOR (7 DOWNT0 0);
OVER_FLOW  :      OUT STD_LOGIC);
END COMPONENT;
```

```
    signal op1 : STD_LOGIC_VECTOR(7 DOWNT0 0);
    signal op2 : STD_LOGIC_VECTOR(7 DOWNT0 0);
SIGNAL RESET      :      STD_LOGIC;
SIGNAL ENTER_OP1   :      STD_LOGIC;
SIGNAL ENTER_OP2   :      STD_LOGIC;
SIGNAL CALCULATE   :      STD_LOGIC;
SIGNAL COMMON_0_OUT :      STD_LOGIC;
SIGNAL COMMON_1_OUT :      STD_LOGIC;
SIGNAL COMMON_2_OUT :      STD_LOGIC;
SIGNAL A_OUT       :      STD_LOGIC;
SIGNAL B_OUT       :      STD_LOGIC;
SIGNAL C_OUT       :      STD_LOGIC;
SIGNAL D_OUT       :      STD_LOGIC;
SIGNAL E_OUT       :      STD_LOGIC;
SIGNAL F_OUT       :      STD_LOGIC;
SIGNAL G_OUT       :      STD_LOGIC;
SIGNAL DP_OUT      :      STD_LOGIC;
SIGNAL CLOCK       :      STD_LOGIC;
SIGNAL DATA_IN    :      STD_LOGIC_VECTOR (7 DOWNT0 0);
SIGNAL OVER_FLOW   :      STD_LOGIC;
```

```
constant CLK_period: time := 1 us;
```

```
constant TC_period: time := 65536 us;
```

BEGIN

UUT: TopLevel PORT MAP(

 RESET => RESET,
 ENTER_OP1 => ENTER_OP1,
 ENTER_OP2 => ENTER_OP2,
 CALCULATE => CALCULATE,
 COMMON_0_OUT => COMMON_0_OUT,
 COMMON_1_OUT => COMMON_1_OUT,
 COMMON_2_OUT => COMMON_2_OUT,
 A_OUT => A_OUT,
 B_OUT => B_OUT,
 C_OUT => C_OUT,
 D_OUT => D_OUT,
 E_OUT => E_OUT,
 F_OUT => F_OUT,
 G_OUT => G_OUT,
 DP_OUT => DP_OUT,
 CLOCK => CLOCK,
 DATA_IN => DATA_IN,
 OVER_FLOW => OVER_FLOW

);

CLK_process : process

begin

 CLOCK <= '1';
 wait for CLK_period/2;
 CLOCK <= '0';
 wait for CLK_period/2;

```
end process CLK_process;
```

```
stim_proc: process
```

```
begin
```

```
RESET <= '1';
```

```
ENTER_OP1 <= '0';
```

```
ENTER_OP2 <= '0';
```

```
CALCULATE <= '0';
```

```
DATA_IN <=(others => '0');
```

```
wait for 2*CLK_period;
```

```
RESET <='0';
```

```
wait for 4*TC_period;
```

```
ENTER_OP1 <='1';
```

```
DATA_IN <= op1;
```

```
wait for 2*TC_period;
```

```
ENTER_OP1 <='0';
```

```
wait for 4*TC_period;
```

```
ENTER_OP2 <='1';
```

```
DATA_IN <= op2;
```

```
wait for 2*TC_period;
```

```
ENTER_OP2 <='0';
```

```
wait for 4*TC_period;
```

```

CALCULATE <= '1';

wait for 8*TC_period;

wait;

end process stim_proc; --1.835 s

END;

```

 


Рис.2 – Дослідження роботи схеми в симуляції

Висновок: На базі стенда Elbert V2 – Spartan 3A FPGA перевірила роботу автомата.